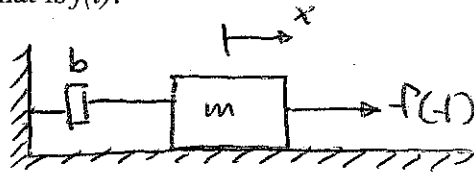





Intake Quiz

These problems should be familiar and a quick review for you. If you cannot solve these problems in under 5 minutes each, take the time to figure out how to solve these and review the material required to do so.

- Write the free body diagram (FBD) and the equations of motion for the following system, assume frictionless surface, dashpot "b," mass "m," and a forcing function that is  $f(t)$ .



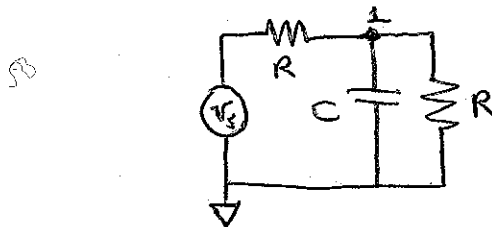- Write down the differential equation for the voltage at node 1, given a voltage source,  $v_s(t)$ . Resistors are valued at  $R$ , and capacitor is valued at  $C$ .



- Given a constant coefficient, linear ordinary differential equation:
  - Find the homogenous or natural solution, given  $y(0) = y_0$ .
  - Find the steady state solution for zero initial conditions and  $u(t)$  is a unit step.
  - Find the full solution, for the above initial conditions and inputs.

$$2\ddot{y} + 3\dot{y} = u$$

$$u = \begin{cases} 1 & t > 0 \\ 0 & t \leq 0 \end{cases}$$

$$y(0) = y_0$$

- Given an ideal op-amp, find  $V_{out}/V_{in}$  for the following configuration:

